

Communicate



Write

1. What materials did you need to make a light bulb light?

2. Which of the diagrams below will make a light bulb light?

3. In your own words, explain how you think a light bulb goes on when it is connected to a battery.



Build On What You Know

The first light bulb was invented by Thomas Edison in 1879. During his life-time, Edison developed 1093 inventions. Two of his inventions are the motion picture camera and the phonograph. Add Edison to your Electric Timeline.